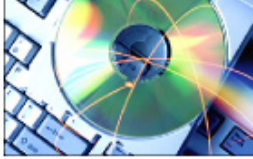


# BECKHOFF



## Application Notes

[www.beckhoffautomation.com](http://www.beckhoffautomation.com)

### **Sensor Wiring Examples for the KL3458 8 Channel 4-20mA Input Module**

KL-AppNote-007

*This application note describes the possible wiring combinations, based on different sensors, with 4 wire, 3 wire, and 2 wire process transmitters.*

2.0

31 October 2007



For additional documentation, please visit

[www.beckhoffautomation.com](http://www.beckhoffautomation.com)

For further assistance, please contact Beckhoff USA support at [supportUSA@beckhoff.com](mailto:supportUSA@beckhoff.com)

Beckhoff Automation  
12150 Nicollet Avenue South  
Burnsville, MN 55337

Phone: + 1 952 / 890 0000

Fax: + 1 952 / 890 2888

[beckhoff.usa@beckhoff.com](mailto:beckhoff.usa@beckhoff.com)



---

# Overview

## Supporting Documents and References

---

[Documentation for KL/KS3458](#)

## Key Concepts and Terms

---

### Concepts


The KL3458 is an eight channel, passive 4-20mA current measurement terminal. It contains an internal shunt that is approximately 65 ohms. It is connected from the input terminal to an internal ground (see data sheet and/or manual). To allow connection signal returns (or to power the 4-20mA loop) the KL9186(24 Vdc) or KL9187(0 Vdc) is required.

### Terms


**Passive:** No external power

**Shunt:** A low value resistance across an A/D converter for changing the 4-20mA current loop to a mV signal

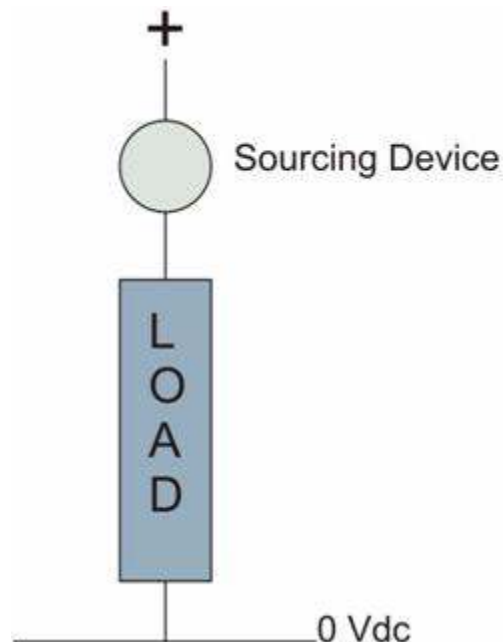**Sourcing:** A device that references the (+) dc power rail



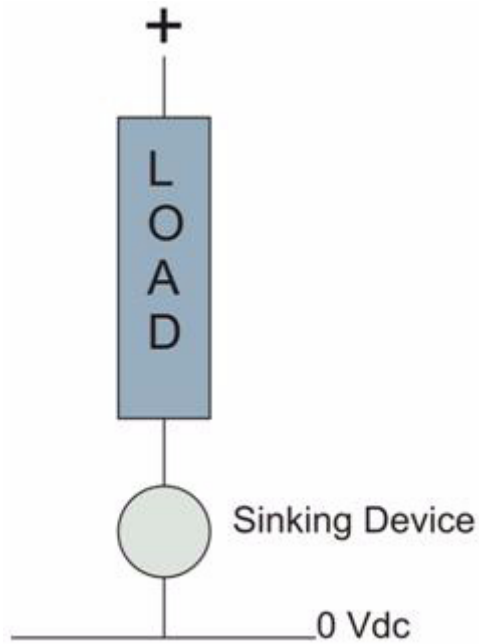**Sinking:** A device that references the (-) dc power rail - 0 Vdc




**Loop Powererd:** General term identifying a 4-20mA loop that needs a dc power supply

**I/O:** Input/Output

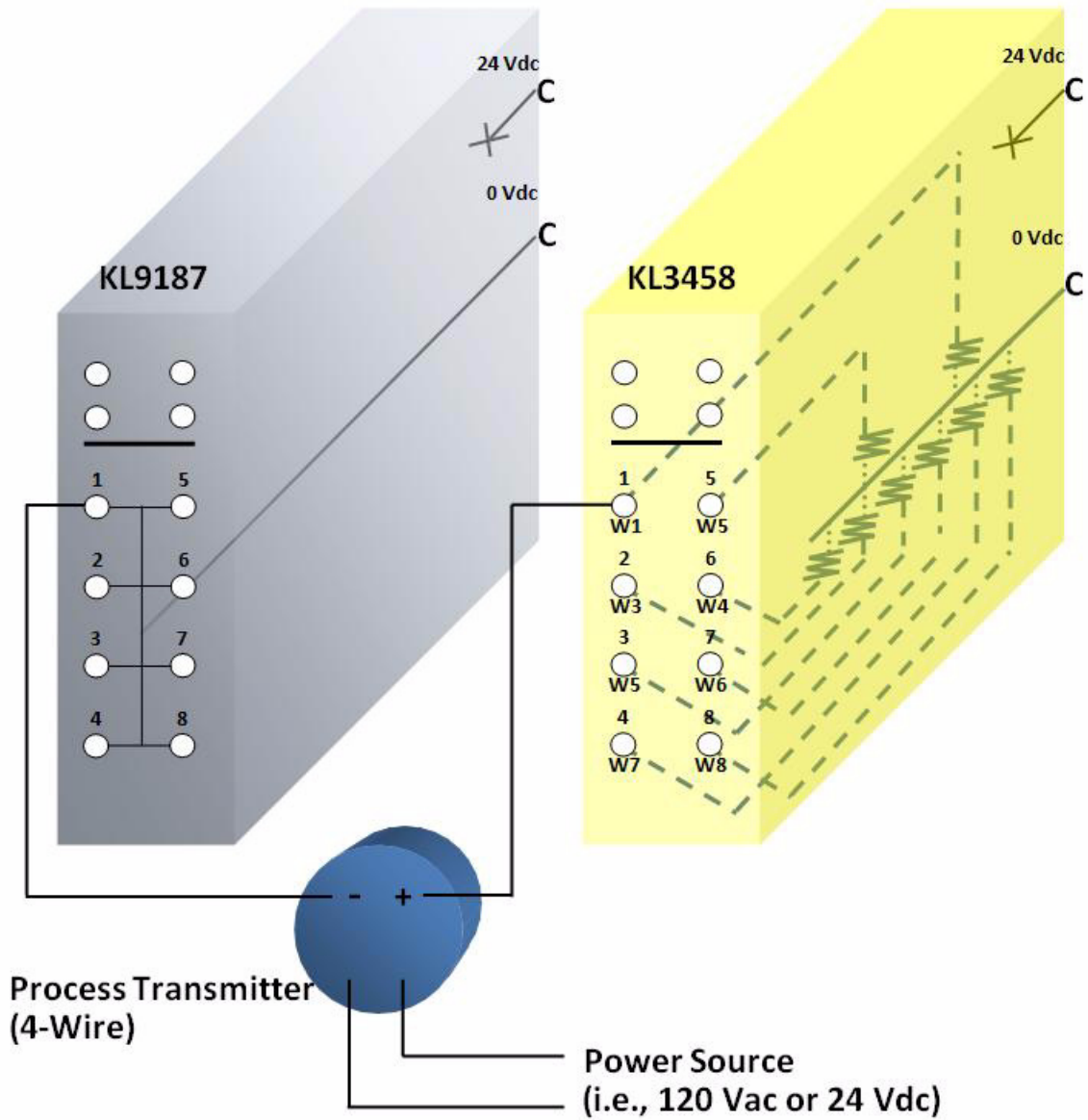**A/D Converter:** Analog to Digital converter. An analog voltage connected at the input of the A/D converter generates a finite digital value at the output of the converter.








---
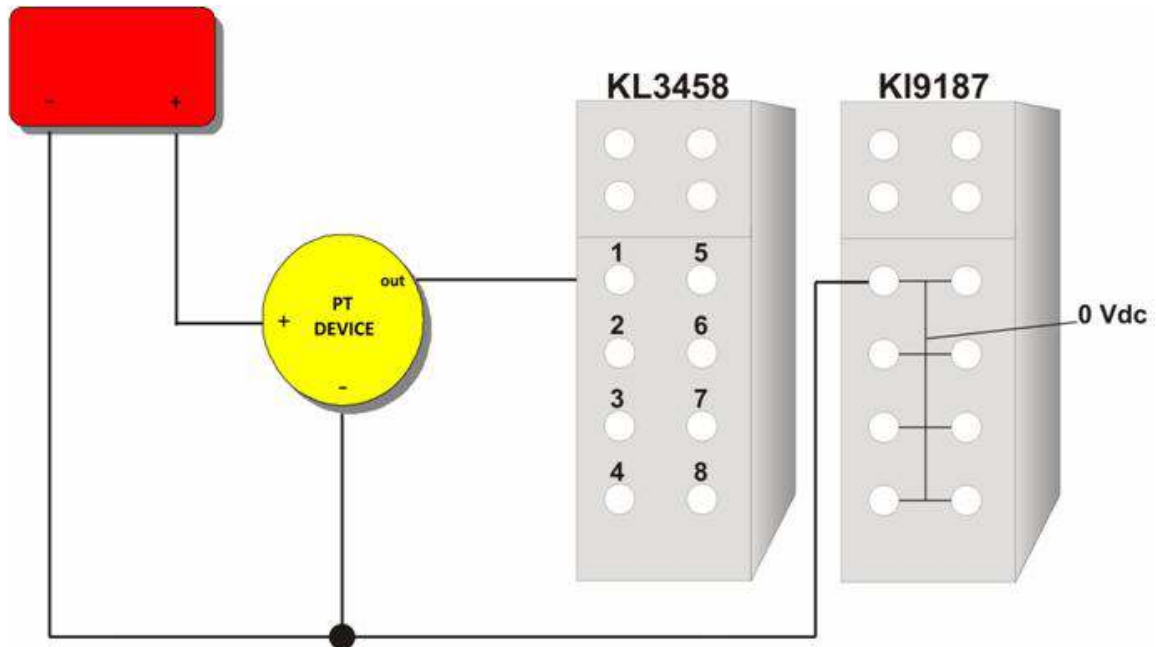
## Example of Loop Power with Multiple 4-20mA Devices

---

The Third diagram is similar to the second, but shows multiple sensor wiring. This DC power supply scheme to supply multiple process transmitters is very common in the industry.



## Conclusion

---

This application note does not include all possible wiring schemes. Innovative ways to land all sensor wires conveniently can be accomplished with the KL9186 and KL9187 terminals.

Please call BUSA technical support at 1-877-TWINCAT with any questions.